



北京大学
PEKING UNIVERSITY

22530007

人工智能与芯片设计

2-Verilog HDL与数字集成电路基础

燕博南
2023秋

Computer Engineering Basics

- Why AI chip?
- Logic Gates? What is computer hardware?
- Flip-Flops? Registers?
- How computer executes program?
- What is GPU?
- Difference between CPU, FPGA, GPU
- <http://www.asic-world.com/verilog/veritut.html>


A good tutorial for open-source simulation:

[全平台轻量开源verilog仿真工具iverilog+GTKWave使用教程](#)

Part 1

Verilog HDL grammar, operators, synthesizable design

Digital Circuit Design Flow

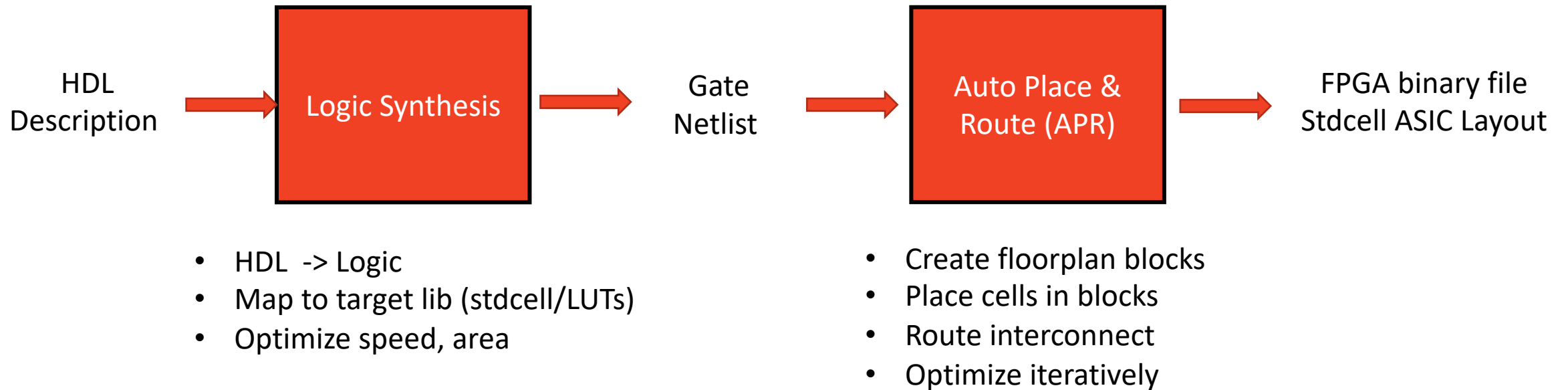

Basic Building - Module

```
1 // single-line comments
2 /* multi-line
3 comments
4 */
5 module name(
6     input a,b,
7     input [31:0] c,
8     output z,
9     output reg [3:0] s
10    ); ← Don't forget ";" here
11 // declarations of internal signals, registers
12 // combinational logic: assign
13 // sequential logic: always @ (posedge clock)
14 // module instances
15 endmodule
```

In Verilog we design modules, one of which will be identified as our top-level module. Modules usually have named, directional ports (specified as `input`, `output`) which are used to communicate with the module.


- Format: HDL ignores space “ ”, it only recognize “;”

Wires & Registers

Wires


```
1 // 2-to-1 multiplexer with dual-polarity outputs
2 module mux2(
3     input a,b,sel,
4     output z,zbar
5 );
6 // again order doesn't matter (concurrent execution!)
7 // syntax is "assign LHS = RHS" where LHS is a wire/bus
8 // and RHS is an expression
9 assign z = sel ? b : a;
10 assign zbar = ~z;
11 endmodule
```

Directly connect!

 

Regs
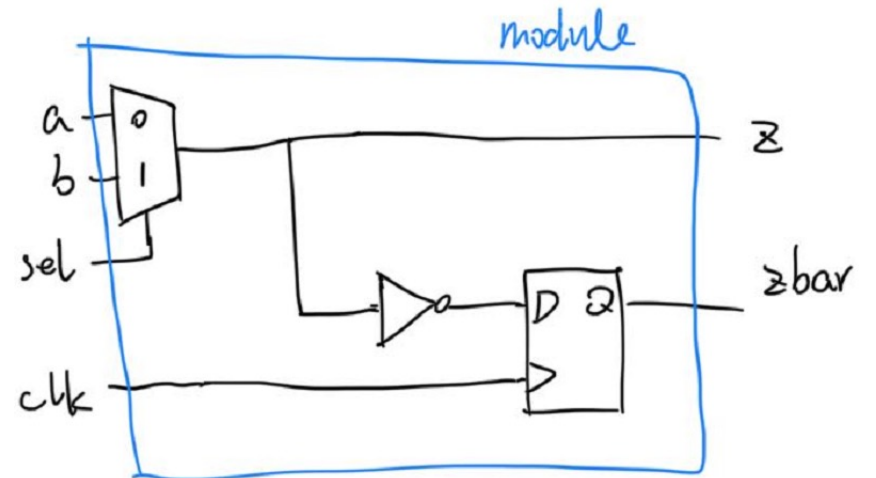
```
1 // 2-to-1 multiplexer with dual-polarity outputs
2 module weird_mux2(
3     input a,b,sel,
4     output z,
5     output reg zbar
6 );
7 // again order doesn't matter (concurrent execution!)
8 // syntax is "assign LHS = RHS" where LHS is a wire/bus
9 // and RHS is an expression
10 assign z = sel ? b : a;
11
12 always @(posedge clk) begin
13     zbar = ~z;
14 end
15
16 endmodule
```



Secrets of Wires & Regs

- Without “reg” declaration, variables are always wires
- Reg can only be output and inside signals
- Assignment:
 - Wires can only be changed using “assign” outside “always”
 - Regs can only be changed inside “always”

```
10 assign zbar = ~z;
```

```
12 always @(posedge clk) begin  
13     zbar = ~z;  
14 end
```

Operators

Arithmetic	*	Multiply
	/	Division
	+	Add
	-	Subtract
	%	Modulus
	+	Unary plus
	-	Unary minus
Logical	!	Logical negation
	&&	Logical and
Relational		Logical or
	>	Greater than
	<	Less than
	>=	Greater than or equal
	<=	Less than or equal
Equality	==	Equality
	!=	inequality
Shift	>>	Right shift
	<<	Left shift
	<<<, >>>	Arithmetic shift

Reduction	~	Bitwise negation
	~&	nand
		or
	~	nor
	^	xor
	^~	xnor
	~^	xnor

Concatenation	{ }	Concatenation
Conditional	?	conditional

What are the difference between (logic) shift and arithmetic shift?

Numeric Constants

Constant values can be specified with a specific width and radix:

123 // default: decimal radix, 32-bit width

'd123 // 'd = decimal radix

1'd3 ??

'h7B // 'h = hex radix

'o173 // 'o = octal radix

is 1'd1

'b111_1011 // 'b = binary radix, “_” are ignored

'hxx // can include X, Z or ? in non-decimal constants

16'd5 // 16-bit constant 'b0000_0000_0000_0101

11'h1X? // 11-bit constant 'b001_XXXX_ZZZZ

By default constants are unsigned and will be extended with 0's on left if need be (if high-order bit is X or Z, the extended bits will be X or Z too).

You can specify a signed constant as follows:



8'shFF // 8-bit twos-complement representation of -1

To be absolutely clear in your intent it's usually best to explicitly specify the width and radix.

Hierarchy: module instances

```
1 // 4-to-1 multiplexer
2 module mux4(input d0,d1,d2,d3, input [1:0] sel, output z);
3   wire z1,z2;
4   // instances must have unique names within current module.
5   // connections are made using .portname(expression) syntax.
6   // once again order doesn't matter...
7   mux2 m1(.sel(sel[0]),.a(d0),.b(d1),.z(z1)); // not using zbar
8   mux2 m2(.sel(sel[0]),.a(d2),.b(d3),.z(z2));
9   mux2 m3(.sel(sel[1]),.a(z1),.b(z2),.z(z));
10  // could also write "mux2 m3(z1,z2,sel[1],z,)" NOT A GOOD IDEA!
11 endmodule
```


- Write all original names (style requirement)
- Connection are concurrently executed

  

Example 1: A counter

```
1 module counter (  
2   out      , // Output of the counter  
3   enable   , // enable for counter  
4   clk      , // clock Input  
5   reset    // reset Input  
6 );  
7  
8 output [1:0] out; //Output Ports  
9 input  enable, clk, reset; //Input Ports  
10  
11 reg [1:0] out; //Internal Variables  
12  
13 always @(posedge clk)  
14 if (reset) begin  
15 | out <= 2'b0 ;  
16 end else if (enable) begin  
17 | out <= out + 1;  
18 end  
19  
20 endmodule
```

What is the timing diagram?

 

- Beware of “before” & “after” clock edge

Verification: Simulation & Testbench


Design:

```
1 module counter (  
2   out      , // Output of the counter  
3   enable   , // enable for counter  
4   clk      , // clock Input  
5   reset    // reset Input  
6 );  
7  
8 output [1:0] out; //Output Ports  
9 input enable, clk, reset; //Input Ports  
10  
11 reg [1:0] out; //Internal Variables  
12  
13 always @(posedge clk)  
14 if (reset) begin  
15 |   out <= 2'b0 ;  
16 end else if (enable) begin  
17 |   out <= out + 1;  
18 end  
19  
20 endmodule
```


Testbench:

```
1 `timescale 1ns/1ps  
2 module Testbench;  
3  
4 wire [1:0] OUT;  
5 reg EN, CLK, RST;  
6  
7 initial CLK = 0;  
8 always #2 CLK=~CLK;  
9  
10 initial begin  
11 |   #1  
12 |   EN = 0;  
13 |   RST = 1;  
14 |   #4  
15 |   EN = 1;  
16 |   RST = 0;  
17 |   #(4*7)  
18 |   EN = 0;  
19 end  
20  
21 counter u1(  
22 .out (OUT)      , // Output of the counter  
23 .enable (EN)   , // enable for counter  
24 .clk (CLK)     , // clock Input  
25 .reset (RST)   // reset Input  
26 );  
27  
28 endmodule
```

Testbench has no ports




Verilog Simulator Workflow

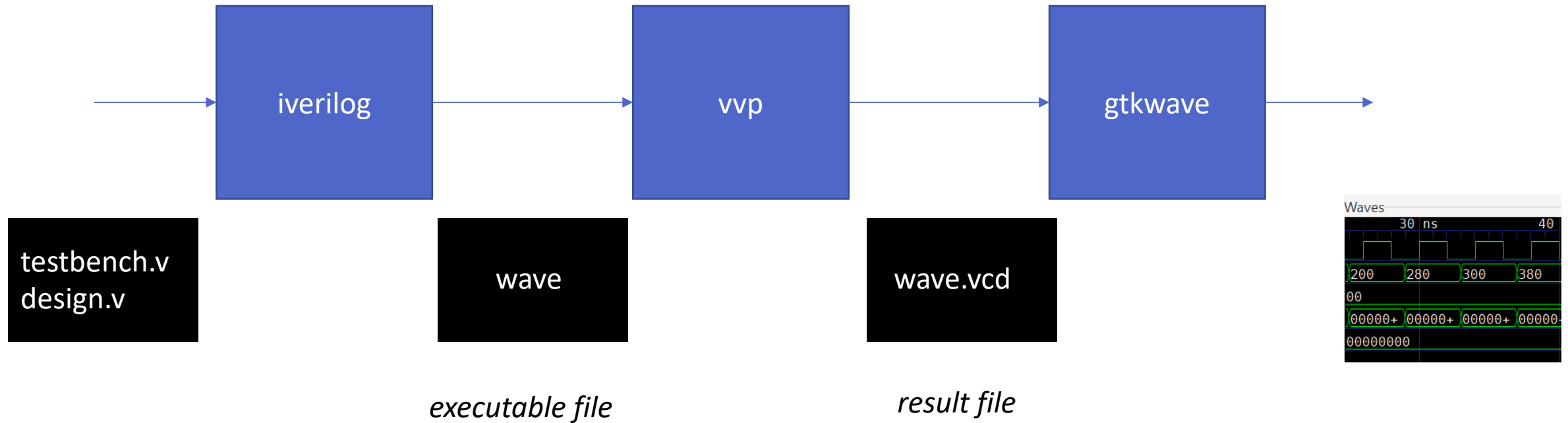

Runnable commend lines:

- 1 `iverilog -o wave testbench.v`
- 2 `vvp -n wave -lxt2`
- 3 `gtkwave wave.vcd -S plot.tcl`


Verilog Simulator Workflow

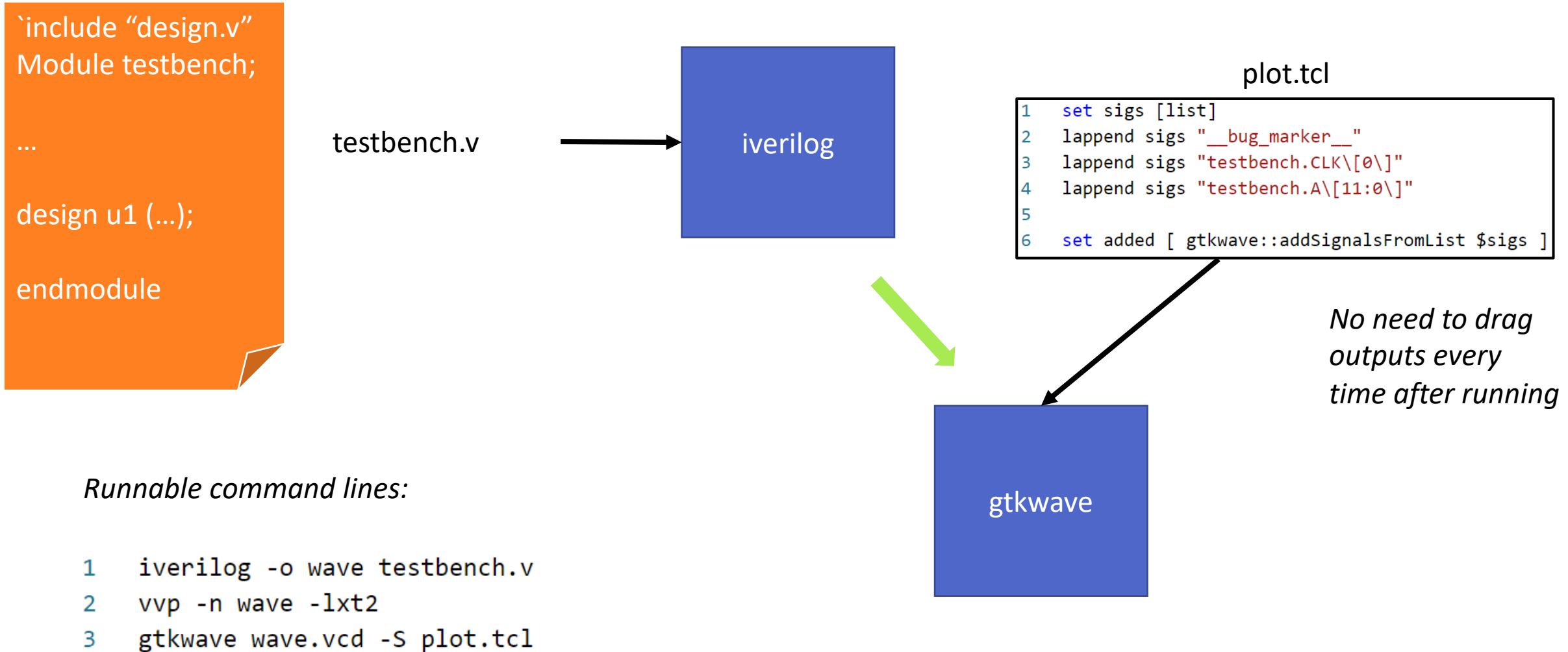

A good tutorial:

[全平台轻量开源verilog仿真工具iverilog+GTKWave使用教程](#)

Blocking and Non-blocking

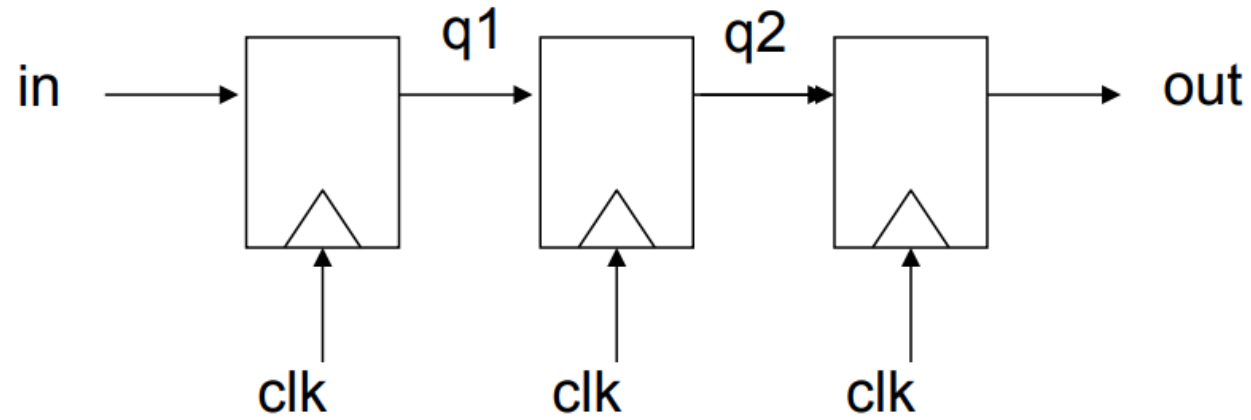

```
1 // shift register
2 reg q1,q2,out;
3 always @(posedge clk) begin
4     q1 = in;
5     q2 = q1;
6     out = q2;
7 end
```

Wrong!

```
1 // shift register
2 reg q1,q2,out;
3 always @(posedge clk) q1 <= in;
4 always @(posedge clk) q2 <= q1;
5 always @(posedge clk) out <= q2;
```



Correct!

Part 2


Finite State Machine

Finite State Machine


- Hardware/Circuits

 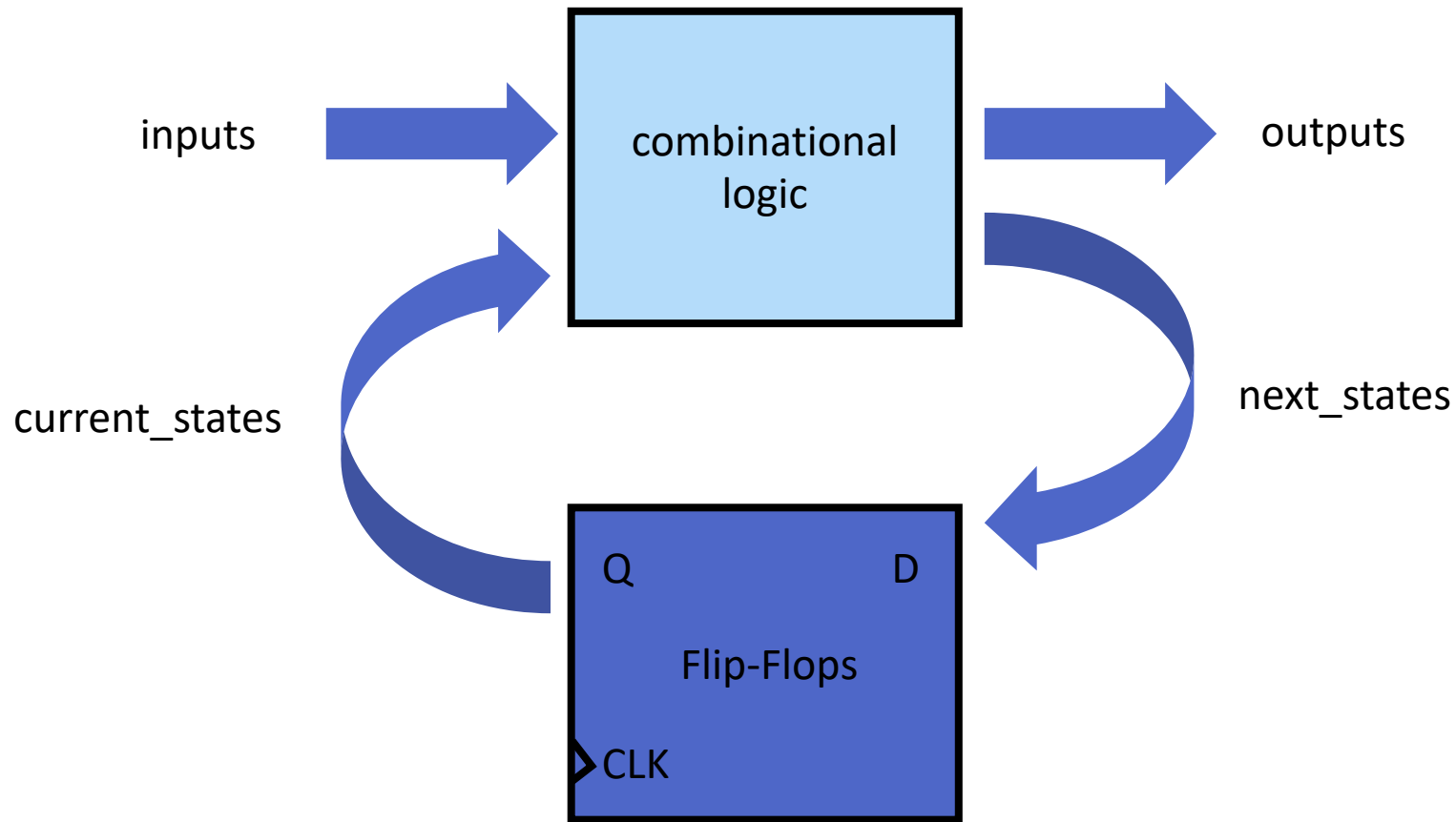

Design Methodologies & Templates

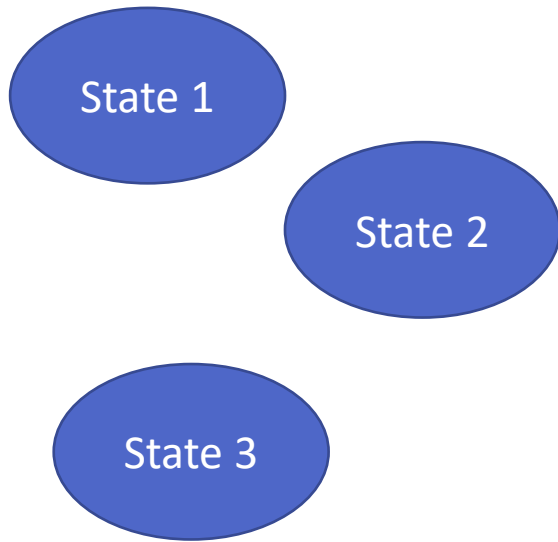

Step 1: define states

 


Step 2: draw state-transfer diagram

```
1 module safe_state_machine (
2     input  clk, data_in, reset,
3     output reg [1:0] data_out
4 );
5
6     reg [1:0] state;
7     // Declare states
8     parameter S0 = 0, S1 = 1, S2 = 2, S3 = 3;
9     // Output depends only on the state
10    always @ (state) begin
11        case (state)
12            S0:
13                data_out = 2'b01;
14            S1:
15                data_out = 2'b10;
16            S2:
17                data_out = 2'b11;
18            S3:
19                data_out = 2'b00;
20            default:
21                data_out = 2'b00;
22        endcase
23    end
24
25    // Determine the next state
26    always @ (posedge clk or posedge reset) begin
27        if (reset)
28            state <= S0;
29        else
30            case (state)
31                S0:
32                    state <= S1;
33            S1:
34                if (data_in)
35                    state <= S2;
36                else
37                    state <= S1;
38            S2:
39                if (data_in)
40                    state <= S3;
41                else
42                    state <= S1;
43            S3:
44                if (data_in)
45                    state <= S2;
46                else
47                    state <= S3;
48            endcase
49    end
```

Step 3: fill in the template

FSM Example 1 Passcode Detector

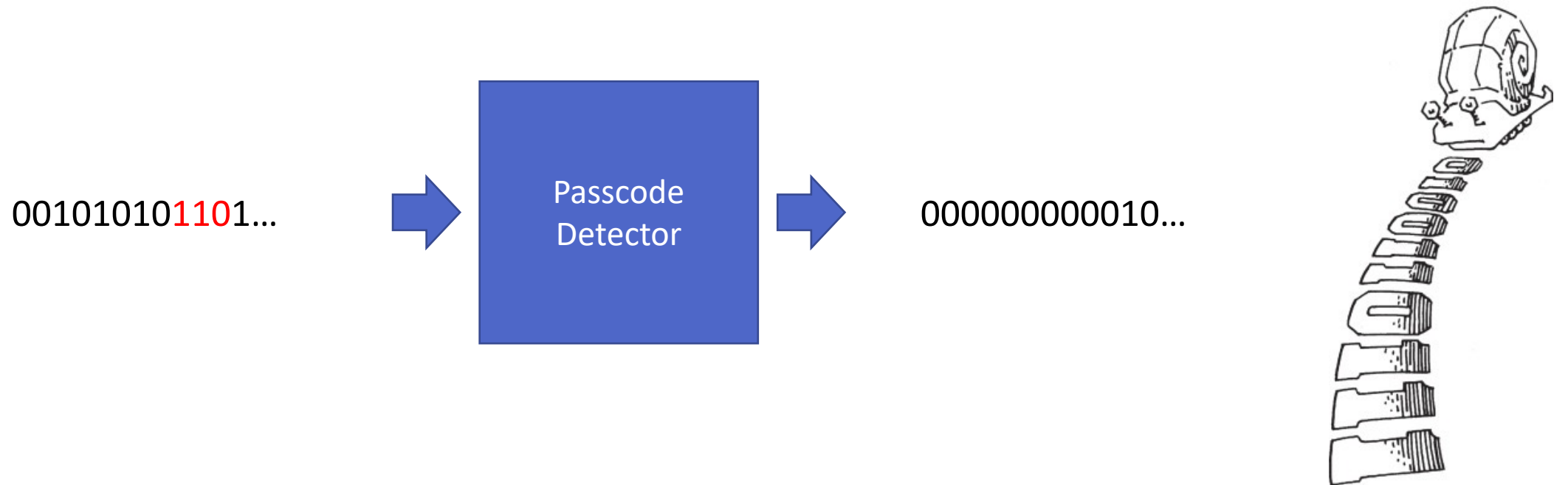
Question: build circuits that outputs 1 pulse, whenever receives "110"



FSM Example 1 – Step 1 & 2

Question: build circuits that outputs 1 pulse, whenever receives “110”

Input: (input, rst**b**)

 

FSM Example 1 – Step 3


Question: build circuits that outputs 1 pulse, whenever receives “110”

```
1  module PasscodeDetector (  
2      input  clk, data_in, rstb,  
3      output reg data_out  
4  );  
5  
6      reg [1:0] state;  
7      // Declare states  
8      parameter STAT_IDLE = 0,  
9              STAT_R1 = 1,  
10             STAT_R2 = 2,  
11             STAT_R3 = 3;  
12     // Output depends only on the state  
13     always @ (state) begin  
14         if(state == STAT_R3) begin  
15             data_out <= 1; // alarming!  
16         end  
17         else begin  
18             data_out <= 0;  
19         end  
20     end
```


```
22     // Determine the next state  
23     always @ (posedge clk) begin  
24         if (~rstb)  
25             state <= STAT_IDLE;  
26         else  
27             case (state)  
28                 STAT_IDLE: begin  
29                     if(data_in==1) begin  
30                         state <= STAT_R1;  
31                     end  
32                 end  
33                 STAT_R1: begin  
34                     if (data_in==1)  
35                         state <= STAT_R2;  
36                     else  
37                         state <= STAT_IDLE;  
38                 end  
39                 STAT_R2: begin  
40                     if (data_in==0)  
41                         state <= STAT_R3;  
42                     else  
43                         state <= STAT_R2;  
44                 end  
45                 STAT_R3: begin  
46                     if(data_in==1) begin  
47                         state <= STAT_R1;  
48                     end  
49                     else begin  
50                         state <= STAT_IDLE;  
51                     end  
52                 end  
53             endcase  
54         end  
55     endmodule
```

FSM Example 2 Auto Chip Testing Environment

 Push button to test Function 1, Function 2, Function 3, ... in series



FSM Example 2 Step 1&2

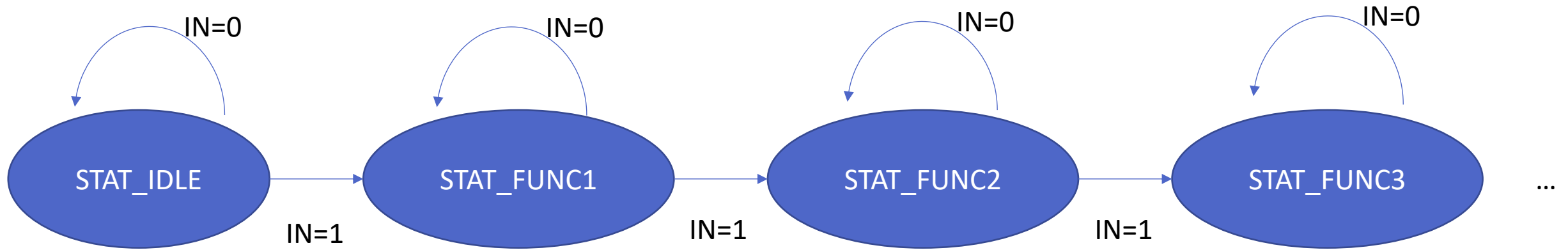

Step 3 is so easy... that you can fill it yourself.

Another Question

Philosophy behind:

Use “state variable” to label timing

Another Q:

How to generate custom waveform
after entering some state?

Solution: setup an counter variable

Do everything at its pace

[! DO NOT ABUSE. This may cause
large comparing logic.]



Possibility of Nested State Machine!

```
1  always @ (posedge clk or posedge reset) begin
2      if (reset)
3          state <= S0;
4      else begin
5          case (state)
6              S0:
7                  data_out = 2'b01;
8              S1: begin
9                  if(cnt==10'd1) begin
10                     //do what you want
11                 end
12                 else if (cnt<=10'd5) begin
13                     //do what you want
14                 end
15                 else if (cnt<=10'd20) begin
16                     //do what you want
17                 end
18                 else begin
19                     //do what you want
20                 end
21             end
22         end
23         S2:
24             data_out = 2'b11;
25         S3:
26             data_out = 2'b00;
27         default:
28             data_out = 2'b00;
29     endcase
30 end
31 end
```


A practical application – Vending Machine

All selections are ¥ 0.30

The machine make changes

Inputs:

- ¥ 0.25
- ¥ 0.10
- ¥ 0.05

Outputs

- Dispense can
- Dispense ¥ 0.10
- Dispense ¥ 0.05



Example from MIT

A practical application – Vending Machine

- A starting (idle) state:

idle

- A state for each possible amount of money captured:

got5c got10c got15c ...

- What's the maximum amount of money captured before purchase?


25 cents (just shy of a purchase) + one quarter (largest coin)

... got35c got40c got45c got50c

- States to dispense change (one per coin dispensed):



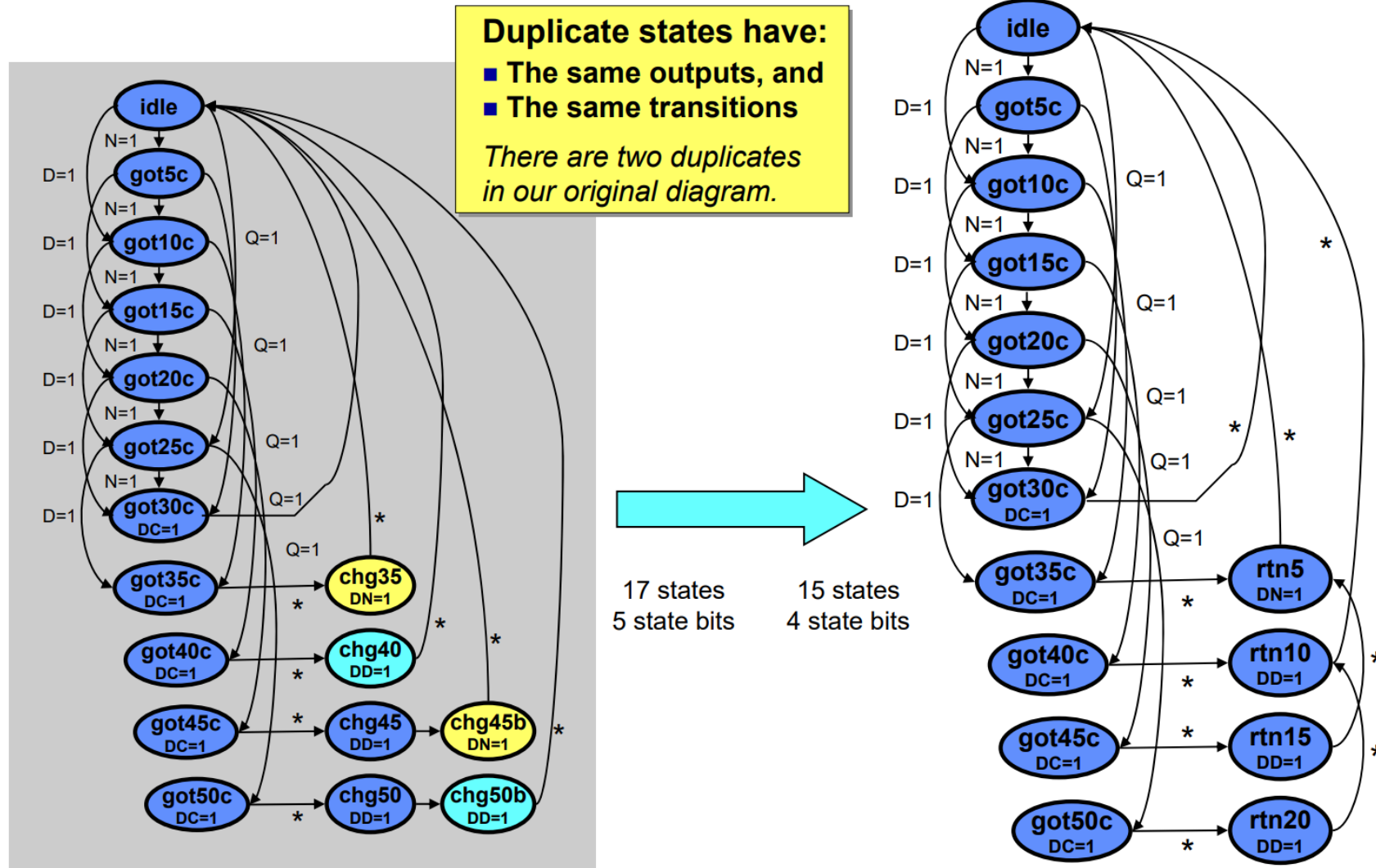A practical application – Vending Machine



Discussion

- State Machine vs. AI
 - State machines exhaustively cover all cases, which is impossible in AI agent design.
- State machine is appropriate for small scale designs.
- Nested state machines:
 - normally, do not nest inside FSM in >2 folds.
 - Otherwise, too complicated **timing path** dependency.